



FreeExams.co.ke

UNIVERSITY EXAMINATIONS
2022/2023 ACADEMIC YEAR

SUPPLEMENTARY/SPECIAL EXAMINATION
YEAR ONE SEMESTER TWO
FOR THE DEGREE
(INFORMATION TECHNOLOGY)

COURSE CODE : **BIT 124**

COURSE TITLE : **DIGITAL ELECTRONICS**

DATE: 10/08/2023 **TIME: 08.00A.M. - 10.00A.M.** **2HRS**

INSTRUCTIONS TO CANDIDATES

ANSWER QUESTIONS ONE AND ANY OTHER TWO.

QUESTION ONE (COMPULSORY)[30 MARKS]

- a. Define the term digital system hence give one example of such a system. [3 marks]
- b. What is a Logic gate? [2 marks]
- c. Draw a truth table and a logic diagram that implements the following function.
 $T(\bar{S}+P)$ [6 marks]
- d. Define a combination logic circuit by outlining its three major attributes. [3 marks]
- e. What is propagation delay? [2 marks]
- f. What is the binary equivalent of the decimal number 368 [3 marks]
- g. Prove that $ABC + ABC' + AB'C + A'BC = AB + AC + BC$ [3 marks]
- h. What is a sequential logic circuit? [2 marks]
- i. What is a flip flop? [2 marks]
- j. Define the term edge-triggering. [2 marks]
- k. Contrast between latch and flip-flop. [2 marks]

QUESTION TWO [20 MARKS]

- a. A computing system performs its calculations based on Boolean algebra. Explain step by step how the computer performs the calculation (45-20) [5 marks]
- b. Simplify $A + BC$ to its Standard Sum of products hence find its min-terms [5 marks]
- c. Minimize the logic function $F(A,B,C,D) = \sum m(1,3,4,5,6,7,9,12,13)$ using Karnaugh map method. [5 marks]
- d. Explain the operation of a BCD to seven segment display hence illustrate its truth table. [5 marks]

QUESTION THREE [20 MARKS]

- a. Draw a JK flip flop and its characteristic table [2 marks]
- b. Outline any four applications of flip flops. [4 marks]
- c. Describe the two basic operations of a state machine. [4 marks]
- d. Draw the symbol of an Exclusive-NOR gate and its truth table. [4 marks]

- e. With the help of a diagram, state and illustrate the three main ways of specifying the function of a combinational logic circuit. [6 marks]

QUESTION FOUR [20 MARKS]

- a. Generate an AND function using a NAND gate topology. [2 marks]
- b. With the help of a diagram, explain how propagation delay is experienced in a ripple counter. [6 marks]
- c. Design a 3-bit binary up counter [12 marks]

QUESTION FIVE [20 MARKS]

- a. Describe two types of propagation delay. [4 marks]
- b. Describe fan-in and fan-out with respect to logic families [4 marks]
- c. Using logic gates, design a decoder with three input lines and only six output lines. [12 marks]