



FreeExams.co.ke

**UNIVERSITY EXAMINATIONS
2022/2023 ACADEMIC YEAR**

**SPECIAL/SUPPLEMENTARY EXAMINATIONS
YEAR THREE SEMESTER TWO EXAMINATIONS**

**FOR THE DEGREE OF
BACHELOR OF SCIENCE COMPUTER SCIENCE**

COURSE CODE : CSC 353E

COURSE TITLE : DIGITAL SYSTEM DESIGN

DATE: 09 /08/2023


TIME: 11.00AM-1.00PM

INSTRUCTIONS TO CANDIDATES

ANSWER QUESTIONS ONE AND ANY OTHER TWO.

QUESTION ONE (COMPULSORY) [30 MARKS]

 - a) Highlight the phases of digital system design (4 marks)
- b) What is meant by the term 'Hardware Descriptive Language?' (2 marks)
- c) Discuss the usage of the following technologies in digital system design. (6 marks)
 - i) Standard cell Application Specific ICs
 - ii) Field Programmable Gate Arrays
 - iii) Custom-chip
- d) Write a VHDL entity and architecture declaration of the circuit below: (7 marks)



- e) Develop a truth table of a process statement below (3 marks)

```

PROCESS ( Sel, x1, x2 )
BEGIN

```

```

    IF Sel = '0' THEN
        f <= x1 ;
    ELSE
        f <= x2 ;
    END IF ;

```

```

END PROCESS

```

- f) Write a VHDL code of a circuit represented by the function below: (8 marks)

$$f(x_1, x_2, x_3) = \sum m(0, 2, 4, 5, 6)$$

SECTION B

QUESTION TWO

- a) Highlight six considerations in the design process (6 marks)
- b) Define the term synthesis in HDL and outline its phases (8 marks)
- c) Write a VHDL code of a circuit represented by the function: (6 marks)

$$f(x_1, x_2) = \bar{x}_1\bar{x}_2 + \bar{x}_1x_2 + x_1x_2$$

QUESTION THREE

- a) Describe the following costs in design (6 marks)
 - i) Non-Recurrent Engineering cost
 - ii) Part-cost
 - iii) Time-to-market cost
- b) Below is a truth table of a 4-to-1 multiplexer which has x0, x1, x2, x3 and s as input signals and f as output signal.

Input, s	Output, f
x0	00

x1	01
x2	10
x3	11

- i) Draw a behavioural view block diagram for the multiplexer (4 marks)
- ii) Write a completed VHDL program that assigns signals using WITH _
SELECT_WHEN clauses (10 marks)

QUESTION FOUR

- a) Distinguish HDL programming from normal software languages (4 marks)
- b) Explain the following terms as used in Gate implementation: (4 marks)
- Noise margin
 - Propagation delay
 - Fan-out
 - Cost of a gate
- c) Write the VHDL code of a 4-to-2 priority encoder using the IF_THEN_ELSE clauses to meet the specification of the truth table below:

(12 marks)

inputs				outputs		
x ₁	x ₂	x ₃	x ₄	y ₁	y ₂	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	x	1	0	1
1	x	x	x	1	1	1

QUESTION FIVE

- a) Describe the details of the following phases; design entry, synthesis, functional simulation, physical design, timing simulation and chip configuration, of a typical Computer Aided Design system for developing the logic circuit (10 marks)
- b) Write a VHDL code for a 2-to-4 decoder using the CASE_WHEN_OTHERS statements to implement the truth table. x₁ and x₂ are the data inputs. En is the enable input (10 marks)

inputs			outputs			
En	x ₁	x ₀	y ₀	y ₁	y ₂	y ₃
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	1	1	0
1	1	1	1	0	0	0
0	x	x	0	0	0	0