



FreeExams.co.ke

**UNIVERSITY EXAMINATIONS  
2022/2023 ACADEMIC YEAR**

**END OF SEMESTER EXAMINATIONS  
SECOND YEARS SEMESTER TWO EXAMINATIONS**

**FOR THE DIPLOMA IN  
(INFORMATION TECHNOLOGY)**

**COURSE CODE : DIT 079**  
**COURSE TITLE : DIGITAL ELECTRONICS**


**DATE: 19/04/2023 TIME: 9.00 A.M. - 11.00A.M. 2HRS**

---

**INSTRUCTIONS TO CANDIDATES**  
**ANSWER QUESTIONS ONE AND ANY OTHER TWO.**

**QUESTION ONE (COMPULSORY) [24 MARKS]**

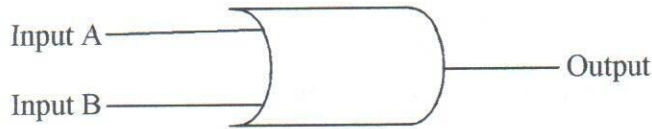
- a) i) Briefly explain the term digitalogics. (2 Marks)  
 ii) State three advantages and one limitation of digital technique when compared to analog technique. (4 Marks)
- b) The diagram shows the symbol for one type of logic gate.



- i) Name the type of gate used. (2 Marks)  
 ii) Draw and complete the truth table of this gate. (4 Marks)
- c) Briefly explain Application of Digital circuits in our industries today (4 Marks)  
 d) Why are digital circuits smaller in size compare to the former analog circuits? (4 Marks)
- e) Convert the following to Binary (2 Marks)  
 i.  $600_{10}$   
 ii.  $(9F2)_{16}$  (2 Marks)

**QUESTION TWO [18 MARKS]**

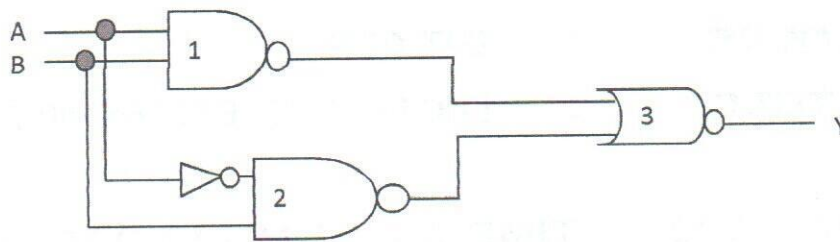- a) What are universal gates? Name two universal gates. (3 Marks)  
 b) Design a logic circuit having three inputs A, B and C which will have its output HIGH only when a majority of the inputs are HIGH. (8 Marks)  
 c) Find the Boolean expression for the logic circuit shown in the figure below. (7 Marks)



Figure

**QUESTION THREE. [18 MARKS]**

- a) i) Express the following equation as sum of product; (3 Marks)  
 $F=A+BC+(A+\bar{C})B$   
 ii) Express the following equation as product of sum; (3 Marks)

$$F = AB + AC + B\bar{C}$$

b) Prove the following theorem  $(Z + X).(Z + \bar{X} + Y) = (Z + X).(Z + Y)$  (6 Marks)

c) Prove De Morgan's theorem for three variables  $\overline{(A+B+C)} = \bar{A} + \bar{B} + \bar{C}$  by filling up a truth table. (6 Marks)

#### QUESTION FOUR [18 MARKS]

a) Solve the following using binary system of numbers using 2's complements : (4 Marks)

i.  $72 - 45 =$

ii.  $45 - 20 =$

b) Evaluate the following division using binary system of numbers : (6 Marks)

i.  $99 \div 11 =$

ii.  $324 \div 27 =$

c) Convert the following numbers without the use of calculator (8 Marks)

i.  $1101_2$  into decimals

ii.  $874_{10}$  into BCD

iii.  $01011110101101010010_2$  into hexadecimal

iv.  $684_{10}$  into hexadecimal

#### QUESTION FIVE [18 MARKS]

a) i. Distinguish between a static and a dynamic memories. (4 Marks)


ii. how many flip flops do you require to store; (4 Marks)

a) 8 byte data

b) 16 kb data

b) What is a logic gate (4 Marks)

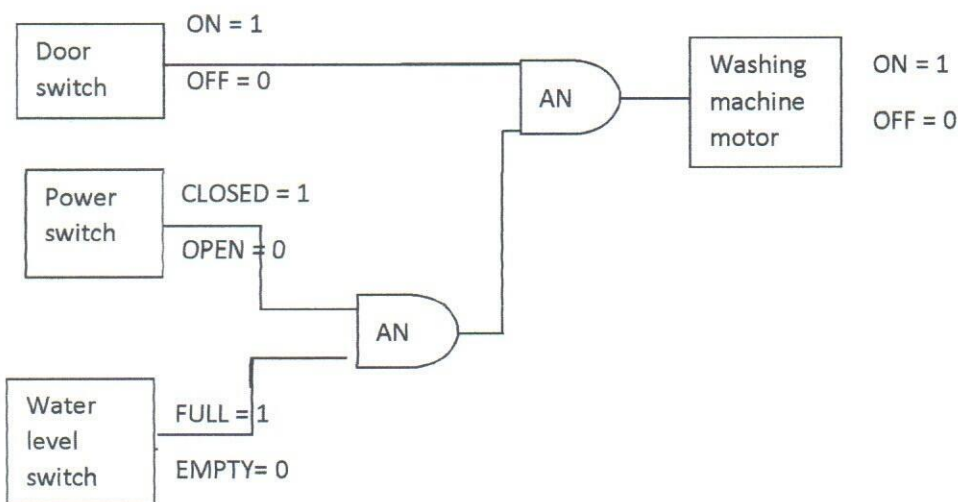c) The diagram shows a control system which may be fitted in an automatic washing machine.



i. Draw and complete a truth table for this control system. (3 Marks)

ii. What conditions will stop the washing machine working? (3 Marks)